

# **UCS704**

# **EMBEDDED SYSTEMS DESIGN**

**Submitted By:**

**Divesh Goel (102103147)**

**COE-5**

**BE-4th Year**



**THAPAR INSTITUTE**  
OF ENGINEERING & TECHNOLOGY  
(Deemed to be University)

**Thapar institute of Engineering and Technology, Patiala**

**June - December 2024**

# INDEX

S no.	Experiment Name	Page No.
1	To study and verify the truth table of various logic gates (NOT, AND, OR, NAND, NOR, EX-OR, & EX-NOR).	3-4
2	To design and verify a half adder using $S = (x+y)(x'+y')$ $C = xy$	4-5
3	To design and verify a full adder using $S = x'y'z + x'yz' + xy'z' + xyz$ $C = xy + xz + yz$	5-6
4	To design and verify a half subtractor using $D = x'y + xy'$ $B = x'y$	6-7
5	Design a BCD to Excess 3 code converter using combinational circuits.	7-8
6	To design and implement a 4:1 multiplexer	8-9
7	To design and implement a 1:4 demultiplexer.	9-10
8	To design and verify a 2:4 decoder.	10-11
9	To design and implement a 4:2 encoder.	11-12
10	To design and verify the operation of D flip-flops using logic gates.	12-13
11	To design and verify the operation of JK flip-flops using logic gates.	13-14

12	To verify the operation of an asynchronous counter.	14-15
----	---	-------

## Experiment 1 (Truth Table and Logic Gates)

To study and verify the truth table of various logic gates (NOT, AND, OR, NAND, NOR, EX-OR, & EX-NOR).

```

module logic_gates;
    reg a, b;
    wire not_a, and_ab, or_ab, nand_ab, nor_ab, xor_ab, xnor_ab;

    not (not_a, a);
    and (and_ab, a, b);
    or (or_ab, a, b);
    nand (nand_ab, a, b);
    nor (nor_ab, a, b);
    xor (xor_ab, a, b);
    xnor (xnor_ab, a, b);

    initial begin
        $display("A B | NOT AND OR NAND NOR XOR XNOR");
        a = 0; b = 0; #1 $display("%b %b | %b %b %b %b %b %b",
        a, b, not_a, and_ab, or_ab, nand_ab, nor_ab, xor_ab,
        xnor_ab);
        a = 0; b = 1; #1 $display("%b %b | %b %b %b %b %b %b",
        a, b, not_a, and_ab, or_ab, nand_ab, nor_ab, xor_ab,
        xnor_ab);
        a = 1; b = 0; #1 $display("%b %b | %b %b %b %b %b %b",
        a, b, not_a, and_ab, or_ab, nand_ab, nor_ab, xor_ab,
        xnor_ab);
        a = 1; b = 1; #1 $display("%b %b | %b %b %b %b %b %b",
        a, b, not_a, and_ab, or_ab, nand_ab, nor_ab, xor_ab,
        xnor_ab);
        a = 1'bX; b = 1'bX; #1 $display("x x | %b %b %b %b",
        not_a, and_ab, or_ab, nand_ab, nor_ab, xor_ab,
        xnor_ab);
    end

```

```
endmodule
```

## Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
A B | NOT AND OR NAND NOR XOR XNOR
0 0 | 1  0  0  1  1  0  1
0 1 | 1  0  1  1  0  1  0
1 0 | 0  0  1  1  0  1  0
1 1 | 0  1  1  0  0  0  1
x x | x  x  x  x  x  x  x
```

## Experiment 2 (Half Adder)

To design and verify a half adder using  $S = (x+y)(x'+y')$   $C = xy$

```
module half_adder;
    reg x, y;
    wire S, C;

    assign S = (x | y) & (~x | ~y);
    assign C = x & y;

    initial begin
        $display("X Y | S C");
        x = 0; y = 0; #1 $display("%b %b | %b %b", x, y, S, C);
        x = 0; y = 1; #1 $display("%b %b | %b %b", x, y, S, C);
        x = 1; y = 0; #1 $display("%b %b | %b %b", x, y, S, C);
        x = 1; y = 1; #1 $display("%b %b | %b %b", x, y, S, C);
        x = 1'b0; y = 1; #1 $display("x %b | %b %b", y, S, C);
    end
endmodule
```

## Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
X Y | S C
0 0 | 0 0
0 1 | 1 0
1 0 | 1 0
1 1 | 0 1
x 1 | x x
```

## Experiment 3 (Full Adder)

To design and verify a full adder using  $S = x'y'z + x'yz' + xy'z' + xyz$

$C = xy + xz + yz$

```
module full_adder;
    reg x, y, z;
    wire S, C;

    assign S = (~x & ~y & z) | (~x & y & ~z) | (x & ~y & ~z) | (x &
y & z);
    assign C = (x & y) | (y & z) | (x & z);

    initial begin
        $display("X Y Z | S C");
        x = 0; y = 0; z = 0; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
        x = 0; y = 0; z = 1; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
        x = 0; y = 1; z = 0; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
        x = 0; y = 1; z = 1; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
```

```

        x = 1; y = 0; z = 0; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
        x = 1; y = 0; z = 1; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
        x = 1; y = 1; z = 0; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
        x = 1; y = 1; z = 1; #1 $display("%b %b %b | %b %b", x, y,
z, S, C);
    end
endmodule

```

### Console Output:

```

C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
X Y Z | S C
0 0 0 | 0 0
0 0 1 | 1 0
0 1 0 | 1 0
0 1 1 | 0 1
1 0 0 | 1 0
1 0 1 | 0 1
1 1 0 | 0 1
1 1 1 | 1 1

```

## Experiment 4 (Half Subtractor)

To design and verify a half subtractor using  $D = x'y + xy'$   $B=x'y$

```

module half_subtractor;
    reg x, y;
    wire D, B;

    assign D = (~x & y) | (x & ~y);
    assign B = ~x & y;

    initial begin
        $display("X Y | D B");
        x = 0; y = 0; #1 $display("%b %b | %b %b", x, y, D, B);
        x = 0; y = 1; #1 $display("%b %b | %b %b", x, y, D, B);
    end
endmodule

```

```

        x = 1; y = 0; #1 $display("%b %b | %b %b", x, y, D, B);
        x = 1; y = 1; #1 $display("%b %b | %b %b", x, y, D, B);
    end
endmodule

```

### Console Output:

```

C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
X Y | D B
0 0 | 0 0
0 1 | 1 1
1 0 | 1 0
1 1 | 0 0

```

## Experiment 5 (Number Converter)

Design a BCD to Excess 3 code converter using combinational circuits.

```

module bcd_to_excess3;
    reg [3:0] bcd;
    wire [3:0] excess3;

    assign excess3 = (bcd <= 4'b1001) ? (bcd + 4'b0011) : 4'bxxxx;

    initial begin
        $display("BCD | Excess-3");
        for (bcd = 4'b0000; bcd <= 4'b1111; bcd = bcd + 1) begin
            #1 $display("%b | %b", bcd, excess3);
        end
    end
endmodule

```

## Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
BCD | Excess-3
0000 | 0011
0001 | 0100
0010 | 0101
0011 | 0110
0100 | 0111
0101 | 1000
0110 | 1001
0111 | 1010
1000 | 1011
1001 | 1100
1010 | xxxx
1011 | xxxx
1100 | xxxx
1101 | xxxx
1110 | xxxx
1111 | xxxx
```

## Experiment 6 (Multiplexer) To design and implement a 4:1 multiplexer

```
module mux_4to1;
    reg [3:0] in;
    reg [1:0] sel;
    wire out;

    assign out = (sel == 2'b00) ? in[0] :
                  (sel == 2'b01) ? in[1] :
                  (sel == 2'b10) ? in[2] :
                  (sel == 2'b11) ? in[3] : 1'bx;

    initial begin
        $display("Sel | Inputs | Out");
        in = 4'b1010;
        for (sel = 0; sel < 4; sel = sel + 1) begin
            #1 $display("%b | %b | %b", sel, in, out);
        end
    end
end
```



```

        sel = 2'bx; #1 $display("x | %b | %b", in, out);
    end
endmodule

```

### Console Output:

```

C:\Users\dives\OneDrive\Documents\embedded>iverilog m.v

C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
Sel | Inputs | Out
00 | 1010 | 0
01 | 1010 | 1
10 | 1010 | 0
11 | 1010 | 1

```

**Experiment 7 (Demultiplexer)** To design and implement a 1:4 demultiplexer.

```

module demux_1to4;
    reg in;
    reg [1:0] sel;
    wire [3:0] out;

    assign out[0] = (sel == 2'b00) ? in : 1'b0;
    assign out[1] = (sel == 2'b01) ? in : 1'b0;
    assign out[2] = (sel == 2'b10) ? in : 1'b0;
    assign out[3] = (sel == 2'b11) ? in : 1'b0;

    initial begin
        $display("Sel In | Out");
        in = 1;
        for (sel = 0; sel < 4; sel = sel + 1) begin
            #1 $display("%b %b | %b", sel, in, out);
        end
    end
endmodule

```

## Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>iverilog md.v

C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
Sel In | Out
00 1 | 0001
01 1 | 0010
10 1 | 0100
11 1 | 1000
```

## Experiment 8 (Decoder) To design and verify a 2:4 decoder.

```
module decoder_2to4;
    reg [1:0] in;
    wire [3:0] out;

    assign out[0] = ~in[1] & ~in[0];
    assign out[1] = ~in[1] & in[0];
    assign out[2] = in[1] & ~in[0];
    assign out[3] = in[1] & in[0];

    initial begin
        $display("In | Out");
        for (in = 0; in < 4; in = in + 1) begin
            #1 $display("%b | %b", in, out);
        end
        #1 $finish;
    end
endmodule
```

## Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>iverilog md2.v
```

```
C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
```

In	Out
00	0001
01	0010
10	0100
11	1000

**Experiment 9 (Encoder)** To design and implement a 4:2 encoder.

```
module encoder_4to2;
    reg [3:0] in;
    reg [1:0] out;

    always @(*) begin
        case (in)
            4'b0001: out = 2'b00;
            4'b0010: out = 2'b01;
            4'b0100: out = 2'b10;
            4'b1000: out = 2'b11;
            default: out = 2'bxx;
        endcase
    end

    initial begin
        $display("In      | Out");
        in = 4'b0001; #1 $display("%b | %b", in, out);
        in = 4'b0010; #1 $display("%b | %b", in, out);
        in = 4'b0100; #1 $display("%b | %b", in, out);
        in = 4'b1000; #1 $display("%b | %b", in, out);
        in = 4'b1010; #1 $display("%b | %b", in, out);
    end
endmodule
```

### Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>iverilog e.v

C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
In      | Out
0001    | 00
0010    | 01
0100    | 10
1000    | 11
1010    | xx
```

**Experiment 10 (Flip-Flops)** To design and verify the operation of D flip-flops using logic gates.

```
module d_flipflop;
    reg D, clk;
    reg Q;

    always @(posedge clk) Q <= D;

    initial begin
        clk = 0;
        D = 0;
        #1 clk = 1; #1 $display("D=%b clk=%b | Q=%b", D, clk, Q);
        D = 1;
        #1 clk = 0; #1 $display("D=%b clk=%b | Q=%b", D, clk, Q);
    end
endmodule
```

### Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>iverilog f.v
```

```
C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
```

```
D=0 clk=1 | Q=0
```

```
D=1 clk=0 | Q=0
```

**Experiment 11 (Flip-Flops )** To design and verify the operation of JK flip-flops using logic gates.

```
module jk_flipflop;
    reg J, K, clk;
    wire Q;
    reg Q_int;

    always @(posedge clk) begin
        if (J & ~K) Q_int <= 1;
        else if (~J & K) Q_int <= 0;
        else if (J & K) Q_int <= ~Q_int;
    end

    assign Q = Q_int;

    initial begin
        clk = 0;
        Q_int = 0;
        $display("J K clk | Q");
        J = 0; K = 0; #1 clk = 1; #1 $display("%b %b %b | %b", J, K,
clk, Q);
        J = 0; K = 1; #1 clk = 0; #1 clk = 1; #1 $display("%b %b %b
| %b", J, K, clk, Q);
        J = 1; K = 0; #1 clk = 0; #1 clk = 1; #1 $display("%b %b %b
| %b", J, K, clk, Q);
        J = 1; K = 1; #1 clk = 0; #1 clk = 1; #1 $display("%b %b %b
| %b", J, K, clk, Q);
    end
endmodule
```

## Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
J K clk | Q
0 0 1 | 0
0 1 1 | 0
1 0 1 | 1
1 1 1 | 0
```

## Experiment 12 (Counter)

To verify the operation of an asynchronous counter.

```
module async_counter(input clk, output reg [3:0] Q);

    initial begin
        Q = 4'b0000;
    end

    always @(posedge clk) begin
        Q <= Q + 1;
    end

endmodule

module async_counter_tb;
    reg clk;
    wire [3:0] Q;
    async_counter uut (.clk(clk), .Q(Q));

    initial begin
        clk = 0;
        $display("Count");
        forever begin
            #5 clk = ~clk;
        end
    end

end
```

```
    initial begin
        forever begin
            #6 $display("%b", Q);
        end
    end
endmodule
```

## Console Output:

```
C:\Users\dives\OneDrive\Documents\embedded>iverilog c.v

C:\Users\dives\OneDrive\Documents\embedded>vvp a.out
Count
0001
0001
0010
0010
0011
0100
0100
0101
0101
0110
0111
0111
1000
1000
1001
1010
1010
1010
1011
1011
1100
1101
1101
1110
1110
1111
0000
```